

## Elektrics & Maths! Internal Training material from [www.EASA66.com](http://www.EASA66.com)

Single modules cost Euro 20 to 70 and can be opened immediately!

1 Ampere is 1 Coulomb per Second =  $6.25 \cdot 10^{18}$  Elektrons per Second.

Please write down that number with all its zeros  $6.25 \cdot 10^{18}$  !

A dry cell battery has 1.5 Volt. A 12 Volt Battery has      cells?

A lead acid accumulator has a nominal voltage per cell of 2.1 Volts. A 24 Volt accumulator has got how many cells      ?

A NiCad-Accumulator has a nominal voltage per cell of 1.25 Volts. A 12 Volt-Accumulator has got how many cells      ?

A NiCad-Accumulator has a constant discharge of 90% of its capacity. A 50Ah Aaccumulator has got how many Ah left?

Ohms law is  $I = \frac{E}{R}$  and the power law is  $P = E \cdot I$  ,

A 115V light with  $30\Omega$  has got a current of      A and a power of      W.

Power is measured in Watt. 1 HP has 746 Watts. 1kW has      HP!

## Elektrics & Maths! Internal Training material from [www.EASA66.com](http://www.EASA66.com)

One Watt is one Joule per Second. 500J/s are \_\_\_\_ Watts and \_\_\_\_ Amperes at 10V.

Voltages in a series circuit:  $V_t = V_1 + V_2 + V_3 + \dots$

$V_t$  is 115V,  $V_1$  is 28V ,  $V_2$  is 55V  $V_3$  is \_\_\_\_ Volt.

Resistances in a series circuit:  $R_t = R_1 + R_2 + R_3 + \dots$

$R_t$  is  $234\Omega$ ,  $R_1$  is  $19\Omega$ ,  $R_2$  is  $123\Omega$ ,  $R_3$  is \_\_\_\_  $\Omega$ .

Currents in a series circuit:  $I_t = I_1 = I_2 = I_3 = \dots$

Voltages in a parallel circuit are everywhere the same!

Currents in a parallel circuit:  $I_t = I_1 + I_2 + I_3 + \dots$

Resistances in a parallel circuit:  $1/R_t = 1/R_1 + 1/R_2 + 1/R_3 + \dots$

In a parallel circuit  $R_1$  is  $5\Omega$ ,  $R_2$  is  $12\Omega$ ,  $R_3$  is  $12\Omega$ .  $R_t$  is \_\_\_\_  $\Omega$ ?

In a parallel circuit  $R_t$  is always smaller than the smallest resistor!!!

Capacitors in a series circuit:  $1/C_t = 1/C_1 + 1/C_2 + 1/C_3 + \dots$

apacitors in a series circuit:  $C_1$  is  $8\mu\text{F}$ ,  $C_2$  is  $7\mu\text{F}$ ,  $C_3$  is  $12\mu\text{F}$ .  $C_t$  ist \_\_\_\_

In a capacitiv series circuit  $C_t$  is always smaller than the smallest capacitor!!!

Capacitors in a parallel circuit: :  $C_t = C_1 + C_2 + C_3 + \dots$

$C_1$  is  $5\mu\text{F}$ ,  $C_2$  is  $7\mu\text{F}$ ,  $C_3$  is  $22\mu\text{F}$ .  $C_t$  is \_\_\_\_

Inductors in a series circuit:  $L_t = L_1 + L_2 + L_3 + \dots$

Inductors in a parallel circuit:  $1/L_t = 1/L_1 + 1/L_2 + 1/L_3 + \dots$

Inductors in a parallel circuit:  $L_1$  is 5mH,  $L_2$  is 3mH,  $L_3$  is 12mH.  $L_t$  is \_\_\_\_

Inductors in a parallel circuit  $C_t$  is always smaller than the smallest inductor!!!

## Elektrics & Maths! Internal Training material from [www.EASA66.com](http://www.EASA66.com)

Single modules cost Euro 20 to 70 and can be opened immediately!

## Transformers

Voltages E of transformers behave like windings N:  $\frac{E_1}{E_2} = \frac{N_1}{N_2}$

The currents of transformers are inversely proportional to their windings N:  $\frac{I_1}{I_2} = \frac{N_2}{N_1}$

## Altenating Current

Peak Voltage = 1.414 x effective Voltage

115V Effektive-Voltage has a peak of \_\_\_\_ V

Average Voltage = 0.636 x peak Voltage

100V average Voltage has a peak of \_\_\_\_ V

Effective Voltage = RMS value = 0.707 x peak Voltage

100V has a Peak of \_\_\_\_ V

Angular frequency "Omega" of an alternating current  $\omega = 2 \pi f$  oder  $\omega = \frac{2\pi}{T}$  Frequency  $f = 1/T$

The energy of a magnetic field of an inductor  $E_{p,m} = \frac{1}{2} B \cdot H \cdot V$  or  $E_{p,m} = \frac{1}{2} L \cdot I^2$

Induced voltage of a moving conductor  $E_{ind}$  equals magnetic density B in Teslar times length of the conductor l in Meter times velocity  $\nu$  in m/s .  $E_{ind} = B \cdot l \cdot \nu$

Alternating Current: Impedance consists of Resistance and Reactance.

$P = E \times I$  is Apparent Power in an A/C circuit  $P = E \times I \times \cos \Phi$  is Real Power

$P = E \times I \times \sin \Phi$  is Reactive Power

500W Apparent Power at  $\cos \Phi$  0,9 has how much Real Power?

500W Apparent Power at  $\sin \Phi$  0,1 has how much Reactive Power?

Power factor in % is the ratio of Real Power to Apparent Power.

Apparent Power KVA ; Real Power in KW ; KVAR Reactive Power = Loss.

500kVA with a **power factor** of 75% has how much Real Power.

## 3-Phase Altenating Current

Voltage Phase to Phase is 1.73 times Voltage Phase to Line  $E = \sqrt{3} \cdot E_{Str}$

## Capacitors

The charge of a capacitor is Capacity x Voltage.  $Q = C \cdot E$

The capacity of a Capacitor is permittivity x area/distance between plates =  $C = \epsilon_D \frac{A}{d}$

A capacitor is blocking Direct Current DC!

English-language power engineering students are advised to remember: "ELI the ICE man" or "ELI on ICE" – the voltage E leads the current I in an inductor L, the current leads the voltage in a capacitor C.

Another common mnemonic is CIVIL – in a capacitor (C) the current (I) leads voltage (V), voltage (V) leads current (I) in an inductor (L).

## Calculating Charging/Discharging of a Capacitor

The Charging Time of a Capacitor depends of Capacitance C and the Resistance R. Therefore the product of Capacitance C and Resistance R is considered as time constant  $\tau$  (tau).  $\tau = R \cdot C$

Within that time constant  $\tau$  (tau) charges or discharges a capacitor about 63% of its applied voltage.

After only 0,69  $\tau$  a capacitor has reached 50% of its final or starting voltage.

**After 5 time constants a capacitor is almost fully charged or discharged!**

The Charging od Discharging time 5  $\tau$ (tau) or 5 times Resistance times Capacity.

